

# Contents

<u>Chapters</u>	<u>Pages</u>
<b>Chapter – 01: Basic Concept of Voltage Regulator</b>	01
1.1. Introduction	01
1.2. Types of Voltage Regulator / Stabilizer	02
1.2.1. Manual Voltage Stabilizer	02
1.2.2. Auto-cut Voltage Stabilizer	03
1.2.3. Automatic Voltage Stabilizer	03
1.2.4. Servo Stabilizer	04
1.3. Different types of Equipments used in the Voltage Regulator/ Stabilizer	05
1.3.1. Switches	05
1.3.2. Meters	05
1.3.3. Indicators	06
1.3.4. Semiconductor Devices	07
1.3.4.1. Diodes	08
1.3.4.2. Transistors	10
1.3.4.3. Thyristors	11
1.3.5. Integrated Circuits	12
<b>Chapter – 02: Relays &amp; Transformers</b>	13
2.1. Introduction	13
2.2. Relay	15
2.2. Construction of Relay	15
2.3. Relay Classification	17
2.4. Relay Operating Speed	18
2.5. Transformer	19
2.6. Types of Transformer	20
2.6.1. Output Voltage	20
2.6.1.1. Step-up Transformer	21
2.6.1.2. Step-down Transformer	21
2.6.2. Core Type	22
2.6.2.1. Permeability	22
2.6.2.2. Electrical Resistivity	22
2.6.3. Usage	22
2.6.3.1. Voltage or Potential Transformer	23
2.6.3.2. Power Transformer	23
2.6.3.3. Current or Series Transformer	23
2.6.3.4. Impedance or Coupling Transformer	23
2.6.3.5. Isolation Transformer	24
2.6.3.6. Auto Transformer	24
2.7. Different Types of Windings	24
2.7.1. Layer Winding	25

2.7.2. Random Winding	25
2.7. 3. Bifilar Winding	25
2.8. Transformer Ratings (Watts/Volt-Ampere)	25
2.9. Applying DC to Transformer	26
2.10. Repairing a Burned/Defective Transformer	27
2.11. Tools required for transformer making	27
2.12. How to varnish the transformer	29
2.13. Chart showing few calculations of transformers with images	30
<b>Chapter – 03: Basic Modules of a Voltage Regulator/ Stabilizer</b>	31
3.1. Introduction	31
3.2. Regulated DC Power Supply	31
3.3. Rectifier Circuit	33
3.3.1. Half Wave Rectifier	33
3.3.2. Full Wave Rectifier	34
3.3.3. Full Wave Bridge Rectifier	35
3.4. Filter Circuit	36
3.4.1. Capacitor filter	36
3.4.2. Inductive Filter (Choke/Coil)	37
3.4.3. Combination Filters	37
3.5. Regulator	39
3.5.1. Zener Regulator	40
3.5.2. Shunt Regulator	41
3.5.3. Series Regulator	42
3.6. Voltage Level Sensors	43
3.7. Voltage Comparators	44
3.7.1. Comparator using a Transistor and a Zener Diode	44
3.7.2. Comparator using Wheatstone bridge	45
3.7.3. Comparator using Op-Amp.	46
3.7.4. CMOS Comparator	48
3.8. Relay Drivers	49
3.8.1. Relay Driver using Single Transistor	49
3.8.2. Relay Driver using Two Transistor (Darlington Pair)	50
3.8.3. Relay Driver using Combination of PNP and NPN Transistor	51
3.8.4. Relay Driver with Inverter Transistor	52
3.9. Relay Chatter Preventer and Hysteresis	52
3.10. Schmitt Trigger	53
3.11. Complementary Schmitt Trigger	54
3.12. Schmitt Trigger from an Op-Amp	55
<b>Chapter – 04: Cutouts and Protective Devices</b>	56
4.1. Introduction	56
4.2. Over Voltage Cutout	56
4.3. Fail Safe Over voltage Cutout	57

4.4. Fail Safe Undervoltage Cutout	58
4.5. Over/Under Voltage cutout using Transistors	58
4.6. Over/Under Voltage cutout using OR Gates	59
4.7. Fail Safe Over/Under Voltage neither Cutouts using NOR Gates	60
4.8. Over Voltage/Under Voltage Cutouts using 1C CD4011	61
4.9. Cutouts Using 1C 747	63
4.10. Cutouts using Op-Amps	64
4.11. Fuse	65
4.11.1. Fast Acting Fuse	65
4.11.2. Slow Blow Fuse	65
4.12. Circuit Breakers	66
4.13. Time Delay Indicator	66
<b>Chapter – 05: Practical Voltage Regulator Circuits: Automatic Voltage Stabilizer</b>	68
5.1. Introduction	68
5.2. Automatic Voltage Stabilizer	68
5.2.1. Automatic Voltage stabilizer using single relay	68
5.3. Schmitt Trigger Stabilizer using Single Relay	70
5.4. Automatic Stabilizer using Separate Sensor & Relay Driver Winding	72
5.5. Buck Boost connections	73
5.6. Buck Boost Operations	74
5.7. Automatic Stabilizer using Two Relays	75
5.8. Automatic Voltage Stabilizers using Two Pole Relays	77
5.9. Automatic Stabilizer TIVICO TA-250	79
5.10. Automatic Stabilizer with Under/Over Voltage Cutout using Two Relay	82
5.11. Philips Two Relay Stabilizer 835/VS	85
5.12. Setting the Stabilizers	86
5.13. Philips Two Relay Automatic Stabilizer 835/VSP.	87
5.14. Three Relay Stabilizers with Over/Under Voltage Cutout	90
5.15. 0.25 KVA Automatic Voltage Stabilizer	93
5.16. Automatic Stabilizer using IC-747	95
<b>Chapter – 06: Main Faults of an Automatic Voltage Stabilizer</b>	97
<b>Conclusion</b>	100
<b>References</b>	101